

$V_{x1}(\text{volt})$	$V_{x2}(\text{volt})$	$V_y(\text{volt})$
0	0	0
0	5	5
5	0	5
5	5	5

Figure 10

2. Specify the logic gate for circuit 6-10

6) NOT gate

7) NOR gate


8) NAND gate

9) AND gate

10) OR gate

CMOS Logic gates

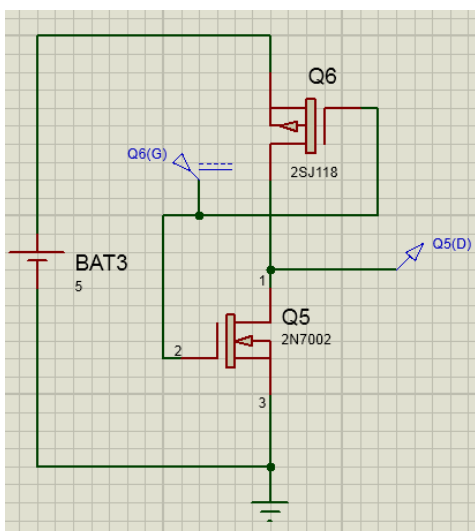1. Implement PMOS logic gate circuits in Figure 11-13, change the values of V_{x1} and V_{x2} according to the table and observe the output V_f .



$V_{x1}(\text{volt})$	$V_f(\text{volt})$
0	5
5	0

Figure 11