


## Lab 7: Sequential Circuit, Memory and Register

### Objectives

- To analyze, design, construct, and test sequential circuits.
- Construct and test a single bit memory and Read-Only Memory(ROM)
- Test dot-matrix display.
 
### Part I: Sequential Circuit Analysis (TTLs required: 7404, 7408, 7432, 7476)

You are to analyze the circuit below. The following steps will help you to learn how to analyze the sequential circuit.



Step 1: Boolean equations for J<sub>1</sub>, K<sub>1</sub>, J<sub>2</sub>, K<sub>2</sub>, and Z.

Step 2: Construct truth tables and K-maps.

Step 3: Construct state tables and state diagram.

Step 4: Sketch timing diagram for the input sequence  $X = 00111100$ .

## Part I: Sequential circuit analysis


You are to analyze the circuit below. The following steps will help you to learn how to analyze the sequential circuit.

**Step 1: Boolean equations** for  $J_1$ ,  $K_1$ ,  $J_2$ ,  $K_2$ , and  $Z$ .

$$J_1 = \underline{x y_2} \quad K_1 = \underline{\bar{x}}$$

$$J_2 = \underline{x} \quad K_2 = \underline{\bar{x} + \bar{y}_1}$$

$$Z = \underline{x y_1 y_2}$$

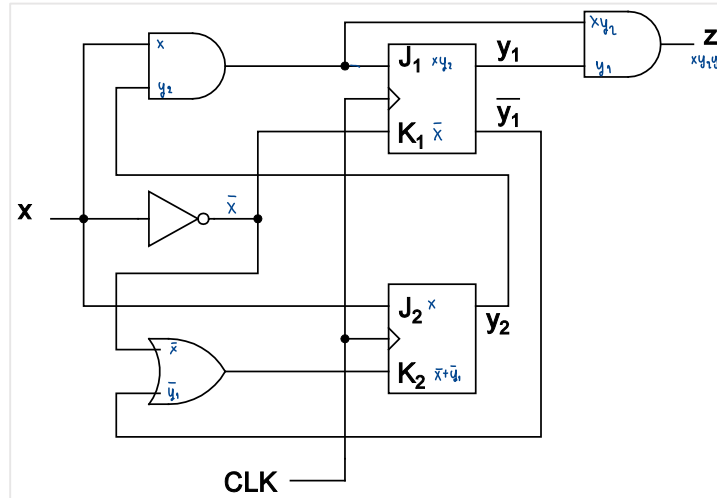

**Step 2: Truth table:**

x	y <sub>1</sub>	y <sub>2</sub>	$J_1$	$K_1$	$J_2$	$K_2$	Z
0	0	0	0	1	0	1	0
0	0	1	0	1	0	1	0
0	1	0	0	1	0	1	0
0	1	1	0	1	0	1	0
1	0	0	0	0	1	1	0
1	0	1	1	0	1	0	0
1	1	0	0	0	1	1	0
1	1	1	1	0	1	0	1

**K-maps:**

$y_1 y_2 \backslash x$	0	1
00	0	0
01	0	1
11	0	1
10	0	0

$J_1$

$y_1 y_2 \backslash x$	0	1
00	1	0
01	1	0
11	1	0
10	1	0

$K_1$

$y_1 y_2 \backslash x$	0	1
00	0	1
01	0	1
11	0	1
10	0	1

$J_2$

$y_1 y_2 \backslash x$	0	1
00	1	1
01	1	0
11	1	0
10	1	1

$K_2$

$y_1 y_2 \backslash x$	0	1
00	0	0
01	0	0
11	0	1
10	0	0

Z


**Step 3: State table:**

$y_1y_2 \backslash x$	0				1			
00	0	1	0	1	0	0	1	1
01	0	1	0	1	1	0	1	0
11	0	1	0	1	1	0	1	0
10	0	1	0	1	0	0	1	1
	$J_1$	$K_1$	$J_2$	$K_2$	$J_1$	$K_1$	$J_2$	$K_2$


$y_1y_2 \backslash x$	0		1	
00	0	0	0	1
01	0	0	1	0
11	0	0	1	1
10	0	0	1	1
	$Y_1$	$Y_2$	$Y_1$	$Y_2$

$y_1y_2 \backslash x$	0	1
00	00/0	01/0
01	00/0	10/0
11	00/0	11/1
10	00/0	11/0
	$Y_1Y_2/z$	

**State diagram**

 

 
**Step 4. Sketch timing diagram for the input sequence  $x = 00111100$ .**



## Part II: Sequential Circuit Design (TTLs required: 7404, 7408, 7432, 7476)

Design a sequential circuit with two JK flip-flops A and B and one input x. When x = 0, the state of the circuit remains the same. When x = 1, the circuit goes through the state transitions from 00 to 01, to 11, to 10, back to 00, and repeats. The output z = 1 when either x = 1 or flip-flop outputs = 11; otherwise z = 0.

Step 1: State diagram:

 

Step 2: Truth table:

i/p	P.S.		N.S.		A		B		o/p
x	y <sub>A</sub>	y <sub>B</sub>	y <sub>A</sub>	y <sub>B</sub>	J <sub>A</sub>	K <sub>A</sub>	J <sub>B</sub>	K <sub>B</sub>	z
0	0	0	0	0	0	x	0	x	0
0	0	1	0	1	0	x	x	0	0
0	1	0	1	0	x	0	0	x	0
0	1	1	1	1	x	0	x	0	1
1	0	0	0	1	0	x	1	x	1
1	0	1	1	1	1	x	x	0	1
1	1	0	0	0	x	1	0	x	1
1	1	1	1	0	x	0	x	1	1

K-maps:

x \ y <sub>A</sub> y <sub>B</sub>	00	01	11	10
0	0	0	x	x
1	0	1	x	x

$$J_A = x y_B$$

x \ y <sub>A</sub> y <sub>B</sub>	00	01	11	10
0	x	x	0	0
1	x	x	0	1

$$K_A = x \bar{y}_B$$

x \ y <sub>A</sub> y <sub>B</sub>	00	01	11	10
0	0	x	x	0
1	x	x	x	0

$$J_B = x \bar{y}_A$$


x \ y <sub>A</sub> y <sub>B</sub>	00	01	11	10
0	x	0	0	x
1	x	0	1	x

$$K_B = x y_A$$

x \ y <sub>A</sub> y <sub>B</sub>	00	01	11	10
0	0	0	1	0
1	0	1	1	1

$$Z = x + y_A y_B$$

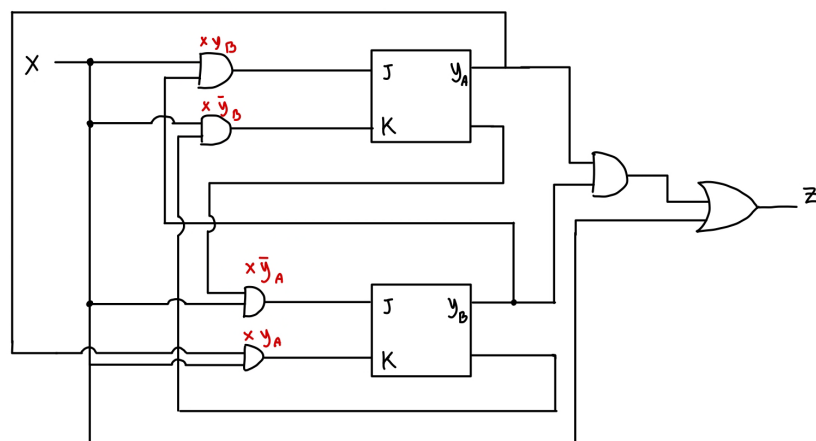Step 4: Circuit Diagram and Proteus simulation:



### Part III: Single-bit memories

#### RAM

Figure 8.1 (a) shows a single-bit memory or a binary cell (BC) shown in Figure 8.1(b). The select input enables the cell for reading or writing, and the  $Read/\overline{Write}$  input determines the operation of the cell when it is selected (or enabled). A “1” in the  $Read/\overline{Write}$  input provides the read operation by forming a path from the latch to the output terminal. A “0” in the  $Read/\overline{Write}$  input provides the write operation by forming a path from the input terminal to the latch.

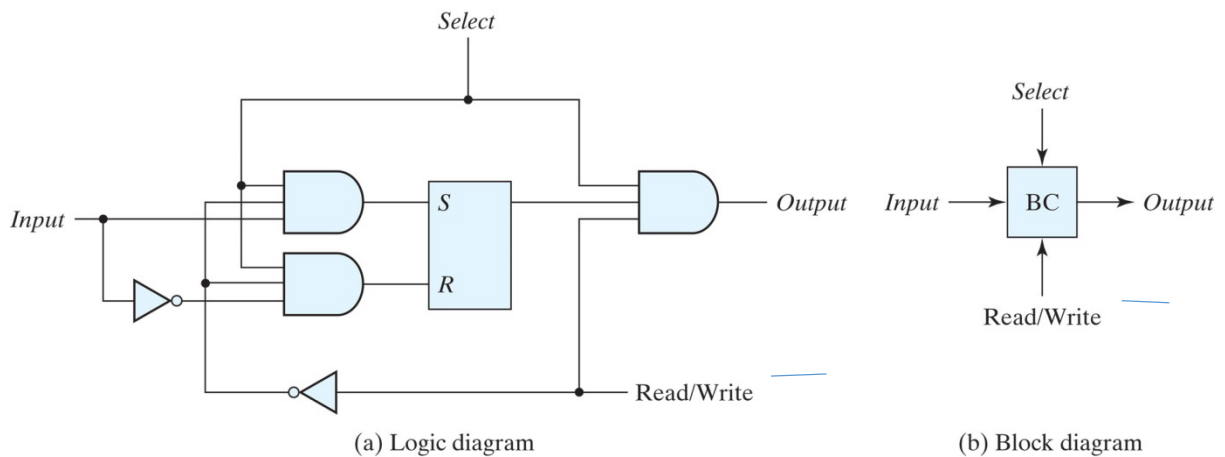



Figure 8.1 Memory cell.

#### ROM


A read-only memory (ROM) is essentially a memory device in which permanent binary information is stored. The binary information must be specified by the designer and is then embedded in the cell.

#### Procedure

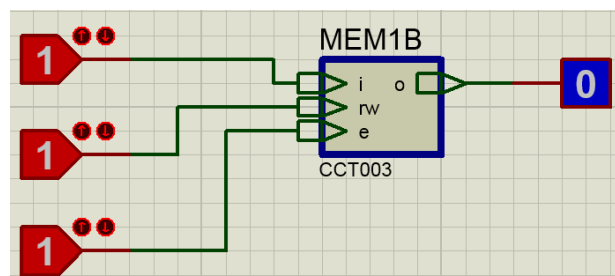1. Use Proteus program to create a single-bit memory cell.



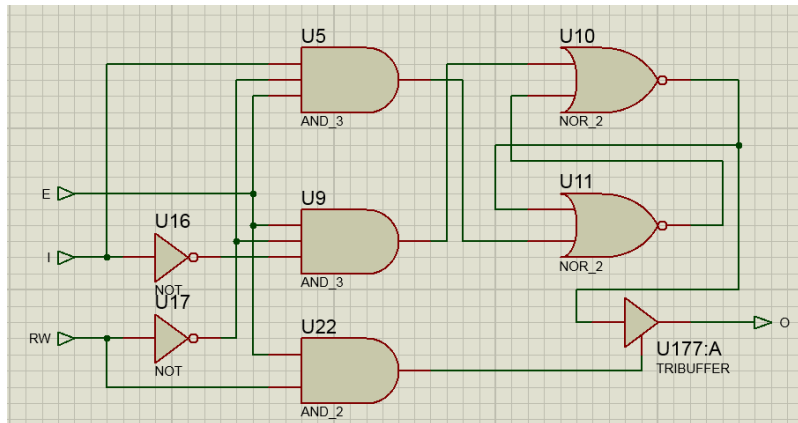I is the input; RW= “1” for “read”, RW= “0” for “write”; E=1 for “enable”; O is the output.



2. Simulate the single-bit RAM and fill in the table 1.

Table 1: RAM

E	RW	I	O	Operation
0	x	x	?	unenable
1	0	0	?	write
1	0	1	?	write
1	1	0	1	read
1	1	1	1	read

3. Build a single bit ROM as shown below. Simulate the read operation and fill in the table


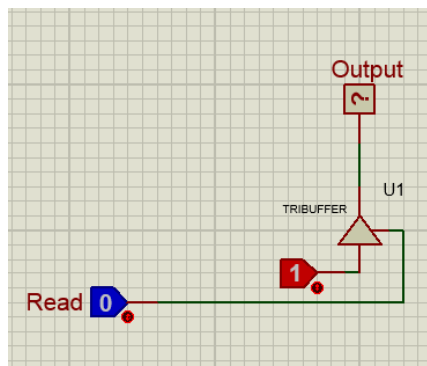


Table 2: ROM

Data	Read	Output	Operation
0	0	?	write
0	1	0	read
1	0	?	write
1	1	1	read

## Part IV: Dot matrix display

 4. Build and test the dot matrix display. Explain how to light up a particular dot at *row-i* and *column-j*.



Explain how to light up a particular dot at row- $i$  and column- $j$

column เมื่อใช้เลข เป็น 1 ไม่ในแถวแนวตั้ง แถวนั้นจะติด และหากใช้เป็น 0 ไม่ในแถวนั้นจะด้วย  
Row เมื่อใช้เลข เป็น 1 ไม่ในแถว แนวนอน จะ ติด แต่ถ้า เป็น 0 ไม่ในแถวนั้น จะ ติด

## Part V: 5x7 ROM

5. Use 2732 ROM chip to build a 5x7 ROM chip driven by the 7493 binary counter. Use input clock B and output QB, QC, and QD as a 3-bit binary counter to count from 0 to 7. Program the ROM so that the dot-matrix display a letter “A”. Show the results to TA.

1 1 0 1 1  
 1 0 1 0 1  
 0 1 1 1 0  
 0 1 1 1 0  
 0 0 0 0 0  
 0 1 1 1 0  
 0 1 1 1 0

ROM  $\rightarrow$     0 | 40    5b    3b    5b | 60 ---

TA Signature: .....