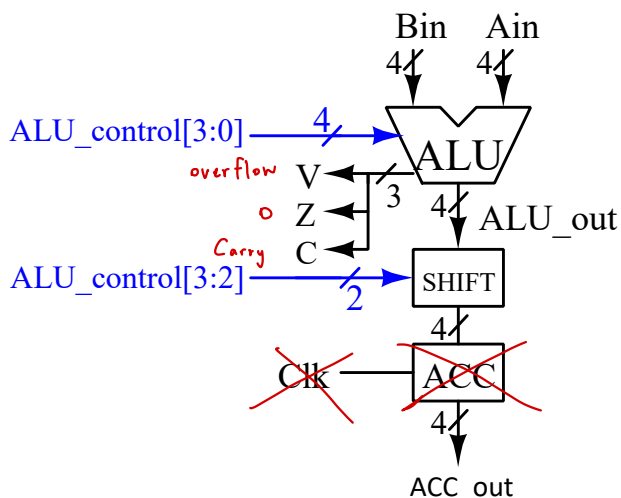


Opcode	Operand	Function	RTN <i>Register Transfer Notation</i>	Mnemonic	Machine code
<del>0000</del>	<del>Address</del>	<del>Load</del>	<del>ACC ← M[Address]</del>	<del>LDA M[Address]</del>	<del>0000 aaaa</del>
<del>0001</del> 0000	Address	Add w/ C	ACC ← ACC + M[Address] + C	ADC M[Address]	0001 aaaa
<del>0010</del>	<del>Address</del>	<del>Subtract w/ C</del>	<del>ACC ← ACC - M[Address] - C</del>	<del>SBC M[Address]</del>	<del>0010 aaaa</del>
<del>0011</del>	<del>Address</del>	<del>Store</del>	<del>M[Address] ← ACC</del>	<del>STA M[Address]</del>	<del>0011 aaaa</del>
<del>0100</del>	xxxx	Clear	ACC ← 0, C ← 0	CLA	0100 xxxx
<del>0101</del> 0001	Address	AND	ACC ← ACC & M[Address]	AND M[Address]	0101 aaaa
<del>0110</del> 0010	Address	OR	ACC ← ACC   M[Address]	OR M[Address]	0110 aaaa
<del>0111</del> 0011	Address	NOT	ACC ← ~ACC	NOT	0111 xxxx
10xx	xxxx	SHL	ACC ← ACC ← 2	SHL	10xx xxxx
11xx	xxxx	SHR	ACC ← ACC ← 2	SHR	11xx xxxx

## Procedure

Design a 4-bit ALU that can perform 10 functions, only the ALU part, not control parts and memories. Implement it on Atrix 7 FPGA board. Use DIP switch as Ain, Bin, and ALU\_control, and LED to display the contents of ACC.



### Example Code

```

module ALU (
    input [3:0] ALU_control, Ain, Bin,
    output reg [3:0] ACC_out,
    output V, Z, C, Clk
);
    wire reg [3:0] ALU_out;

    // write your code here

endmodule

```

TA Signature: Lab11-2A-G4, G8.....

6/11/63